

EE121  
John Wakerly  
Lecture #1




Introduction, Logic Circuits

Administrative

- Handouts
  - Lab Sign-Up Sheet
  - Fact Sheet
  - Course Outline (readings due **before** lecture)
  - Lab Assignment #0 (due next Friday 10/1)
- Turn in Lab Sign-Up Sheet today or Tuesday
- Subscribe to newsgroup “ee121@leland”
- Grading
  - 65-70% labs; do prelabs on-time and do a good job on documentation.
  - midterm + final (equal weight)
  - all labs and exams required; no incompletes.

  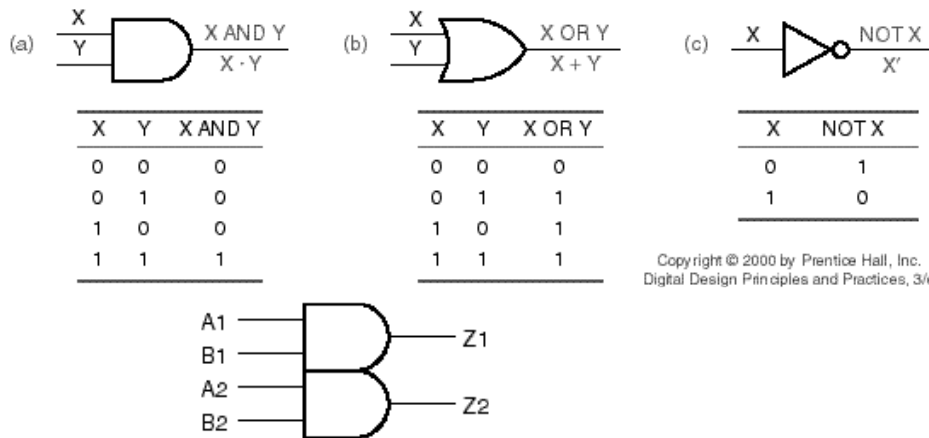
## Digital Logic

- Binary system -- 0 & 1, LOW & HIGH, negated and asserted.
- Basic building blocks -- AND, OR, NOT



## Many representations of digital logic

- Transistor-level circuit diagrams

 


- Gate symbols (for simple elements)


- Truth tables

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- Logic diagrams

 

 - Prepackaged building blocks, e.g. multiplexer



- Equations:  $Z = S' \cdot A + S \cdot B$

- Various hardware description languages
  - ABEL

```

module chap1mux
title 'Two-input multiplexer example'
CHAP1MUX device 'P16V8'

A, B, S      pin 1, 2, 3;
Z            pin 13 istype 'com';

equations

WHEN S == 0 THEN Z = A; ELSE Z = B;

end chap1mux

```

- VHDL

```

library IEEE;
use IEEE.std_logic_1164.all;

entity Vchap1mux is
  port ( A, B, S: in  STD_LOGIC;
         Z:      out STD_LOGIC );
end Vchap1mux;


architecture Vchap1mux_arch of Vchap1mux is
begin
  Z <= A when S = '0' else B;
end Vchap1mux_arch;

```


- We'll start with gates and work our way up
 
## Logic levels

- Undefined region is inherent
  - digital, not analog
  - amplification, weak => strong
- Switching threshold varies with voltage, temp, process, phase of the moon
  - need “noise margin”
- The more you push the technology, the more “analog” it becomes.
- Logic voltage levels decreasing with process
  - 5 -> 3.3 -> 2.5 -> 1.8 V




## MOS Transistors

 

Voltage-controlled resistance


PMOS

 

Voltage-controlled resistance:  
decrease  $V_{gs}$  ==> decrease  $R_{ds}$

Note: normally,  $V_{gs} \leq 0$


NMOS

 

Voltage-controlled resistance:  
increase  $V_{gs}$  ==> decrease  $R_{ds}$

Note: normally,  $V_{gs} \geq 0$

# CMOS Inverter

 



Copyright © 2000 by Prentice Hall, Inc.  
Digital Design Principles and Practices, 3/e

(b)


$V_{IN}$	$Q1$	$Q2$	$V_{OUT}$
0.0 (L)	off	on	5.0 (H)
5.0 (H)	on	off	0.0 (L)



## Switch model

  


## Alternate transistor symbols

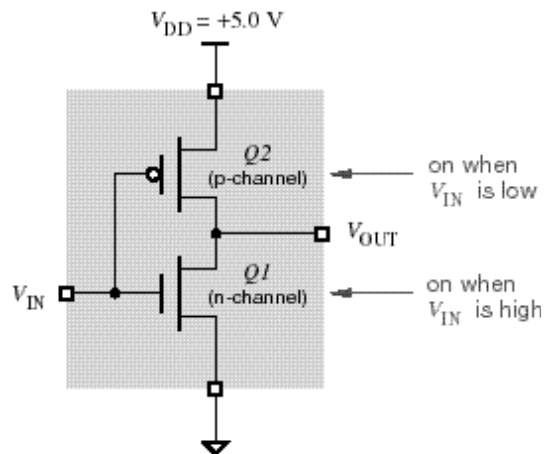
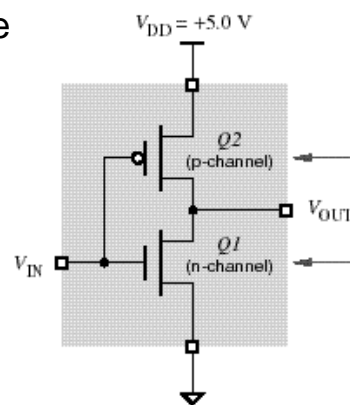
## CMOS Gate Characteristics

- No DC current flow into MOS gate terminal
  - However gate has capacitance  $\Rightarrow$  current required for switching ( $CV^2f$  power)
- No current in output structure except during switching
  - Both transistors partially on
  - Power consumption related to frequency
  - Slow input-signal rise times  $\Rightarrow$  more power
- Symmetric output structure  $\Rightarrow$  equally strong drive in LOW and HIGH states



- E102E announcement
- Foundation demo
- Sign up for mailing list, ee121@leland !
- Turn in lab sign-up sheet by Tuesday!